

Experiment 2

Sequential Synthesis and FPGA Programming

Mohammad
Mahdi
Abdolhosseini,
810198434

Homayoun
Mohseni,
810198464

Abstract— This experiment has two goals: 1. To teach us about state machines that control devices. 2. To introduce us to FPGA devices and how to use them. We will learn about state machines, sequence detectors, Huffman coding, design simulation, synthesis, and FPGA programming through this experiment.

1. SERIAL TRANSMITTER

In this experiment, we designed a circuit that began transmitting data from serIn to serOut when it detected the start sequence "110101" on serIn. The circuit then transmitted whatever appeared on serIn for the next 10 clock cycles, and the serOutvalid was active during this time. After transmitting 10 bits, the circuit returned to the search state for the start sequence.

1.1 ONE-PULSER

One-pulser module provided a clock-enable input for the counter and the sequence detector. We used a push-button on our board (clkPB) to create a single pulse that synchronized with the system clock. The output of the One-Pulser module connected to the clock enable input (clkEn) of the sequence detector and the counter. We wrote the Verilog description of the One-pulser module and tested our design in Modelsim.

One-pulser general structure is shown in figure 1.

The state machine is shown in figure 2 and Quartus generated state machine and transition conditions is shown in figure 3 and 4 respectively.



Fig.1 One-pulser module

 


Fig.2 One-pulser state machine

 


Fig.3 One-pulser Quartus generated state machine

	Source State	Destination State	Condition
1	A	B	(in_pulse)
2	A	A	(!in_pulse)
3	B	C	
4	C	C	(in_pulse)
5	C	A	(!in_pulse)

Fig.4 One-pulser Quartus generated state machine transition conditions

 


Fig.5 One-pulser simulation

1.2 ORTHOGONAL FINITE STATE MACHINE

By designing an Orthogonal FSM using a Moore state machine and a counter, the sequence detector checks for the sequence "110101" on its serIn input and activates the serOutValid output for 10 consecutive clock cycles. We designed the Moore state machine, wrote the Verilog

descriptions for the transmitter circuit, and tested its correctness using a testbench in ModelSim.

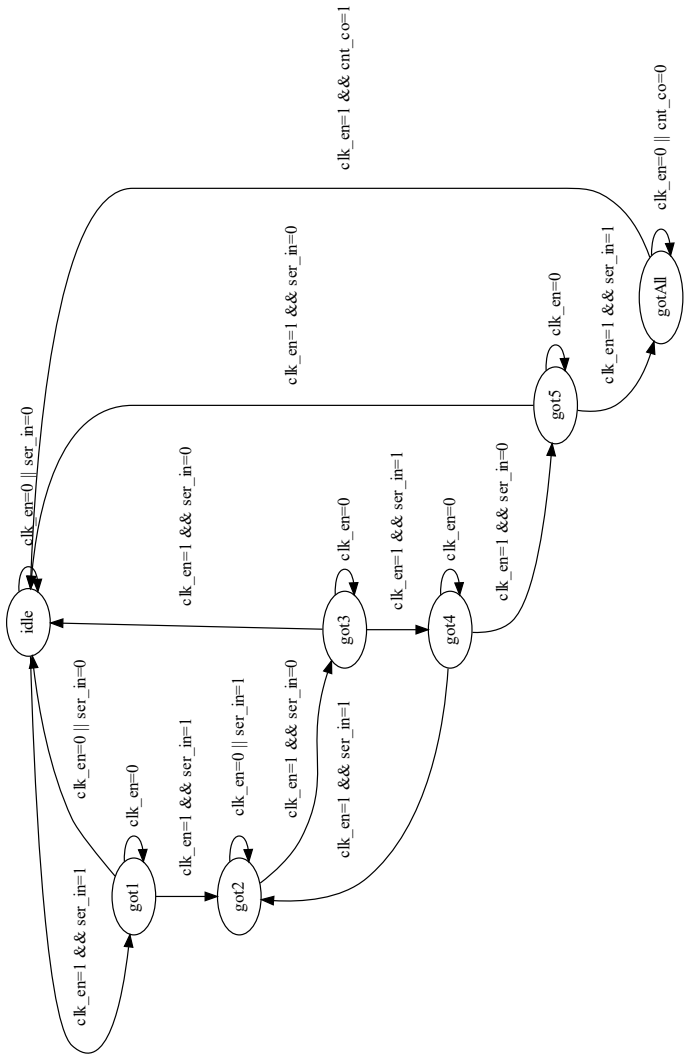


Fig.6 110101 Moore FSM

 


Fig.7 110101 detector module

 


Fig.8 counter internal structure

 


Fig.9 Quartus generated 110101 state machine

	Source State	Destination State	Condition
1	got1	got1	(!clk_en)
2	got1	idle	(clk_en),(ser_in)
3	got1	got2	(ser_in),(clk_en)
4	got2	got3	(clk_en),(!ser_in)
5	got2	got2	(!ser_in),(!clk_en) + (ser_in)
6	got3	got3	(!clk_en)
7	got3	idle	(clk_en),(!ser_in)
8	got3	got4	(clk_en),(ser_in)
9	got4	got5	(clk_en),(!ser_in)
10	got4	got4	(!clk_en)
11	got4	got2	(ser_in),(clk_en)
12	got5	gotAll	(clk_en),(ser_in)
13	got5	got5	(!clk_en)
14	got5	idle	(clk_en),(!ser_in)
15	gotAll	gotAll	(!cnt_co) + (cnt_co),(!clk_en)
16	gotAll	idle	(cnt_co),(clk_en)
17	idle	got1	(clk_en),(ser_in)
18	idle	idle	(!clk_en) + (clk_en),(!ser_in)

Fig.10 Quartus generated 110101 state machine transition conditions

 


Fig.11 Orthogonal FSM wave form

1.3 SEVEN SEGMENT DISPLAY

We designed a display module to show the counter output on seven segment component of the FPGA board. Each seven segment receives a 4-bit input and displays the corresponding HEX value on its 7-bit output.

 


Fig.12 top level circuit including the seven segment component

DESIGN SYNTHESIS AND FPGA PROGRAMMING:

2. SERIAL TRANSMITTER IMPLEMENTATION

For this part, we used the DE1 development board (shown in figure 3) to implement our design. We created a top-level Verilog description that connected the One-pulser, sequence detector, and seven segment display modules together.


 


Fig.3 FPGA board

To begin, we made a Quartus project and added the top-level Verilog codes. We connected the main FPGA clock to the circuit's clock input and added a push-button to the serIn of the serial transmitter circuit and another to the input of the one-pulser circuit.

Afterwards, we performed synthesis and programmed the Cyclone II device. For output display, we used an output LED for displaying serOutvalid and one LED for serOut. We used one seven segment for displaying the counter output.

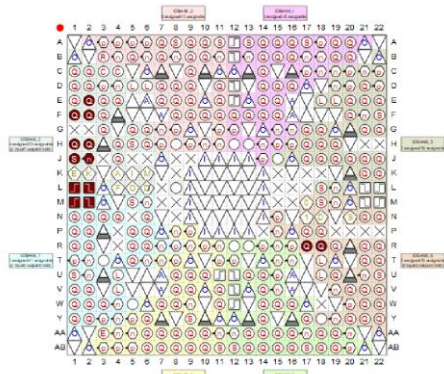
Top View - Wire Bond Cyclone II - EP2C20F484C7



Node Name	Direction	Location	I/O Bank	VREF Group	Filter Location
clk	Input	PIN_L1	2	B2_N1	PIN_L1
in_pulse	Input	PIN_L2	2	B2_N1	PIN_L2
rst	Input	PIN_M2	1	B1_N0	PIN_M2
seq0	Output	PIN_J2	2	B2_N1	PIN_J2
seq1	Output	PIN_J1	2	B2_N1	PIN_J1
seq2	Output	PIN_H2	2	B2_N1	PIN_H2
seq3	Output	PIN_H1	2	B2_N1	PIN_H1
seq4	Output	PIN_F2	2	B2_N1	PIN_F2
seq5	Output	PIN_F1	2	B2_N1	PIN_F1
seq6	Output	PIN_E2	2	B2_N1	PIN_E2
ser_in	Input	PIN_M1	1	B1_N0	PIN_M1
ser_out	Output	PIN_R18	6	B6_N0	PIN_R18
ser_out_valid	Output	PIN_R17	6	B6_N1	PIN_R17

Type	ID	Message
Warning	332148	Timing requirements not met
Warning	332146	Worst-case setup slack is -1.483
Warning	332146	Worst-case hold slack is 0.445
Warning	332140	No Recovery paths to report
Warning	332140	No Removal paths to report
Warning	332146	Worst-case minimum pulse width slack is -1.631
Warning	332001	The selected device family is not supported by the report_metastability command.
Warning	332148	Timing requirements not met
Warning	332146	Worst-case setup slack is -0.023
Warning	332146	Worst-case hold slack is 0.215
Warning	332140	No Recovery paths to report
Warning	332140	No Removal paths to report
Warning	332146	Worst-case minimum pulse width slack is -1.380
Warning	332001	The selected device family is not supported by the report_metastability command.
Warning	332102	Design is not fully constrained for setup requirements
Warning	332102	Design is not fully constrained for hold requirements
Message	293000	Quartus II 64-Bit TimeQuest Timing Analyzer was successful. 0 errors, 4 warnings
Message	293000	Quartus II Full Compilation was successful. 0 errors, 14 warnings

Flow Summary	
Flow Status	Successful - Tue Apr 18 14:13:13 2023
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	serial_transmitter
Top-level Entity Name	serial_transmitter
Family	Cyclone II
Device	EP2C20F484C7
Timing Models	Final
Total logic elements	28 / 18,752 (< 1 %)
Total combinational functions	28 / 18,752 (< 1 %)
Dedicated logic registers	13 / 18,752 (< 1 %)
Total registers	13
Total pins	13 / 315 (4 %)
Total virtual pins	0
Total memory bits	0 / 239,616 (0 %)
Embedded Multiplier 9-bit elements	0 / 52 (0 %)
Total PLLs	0 / 4 (0 %)

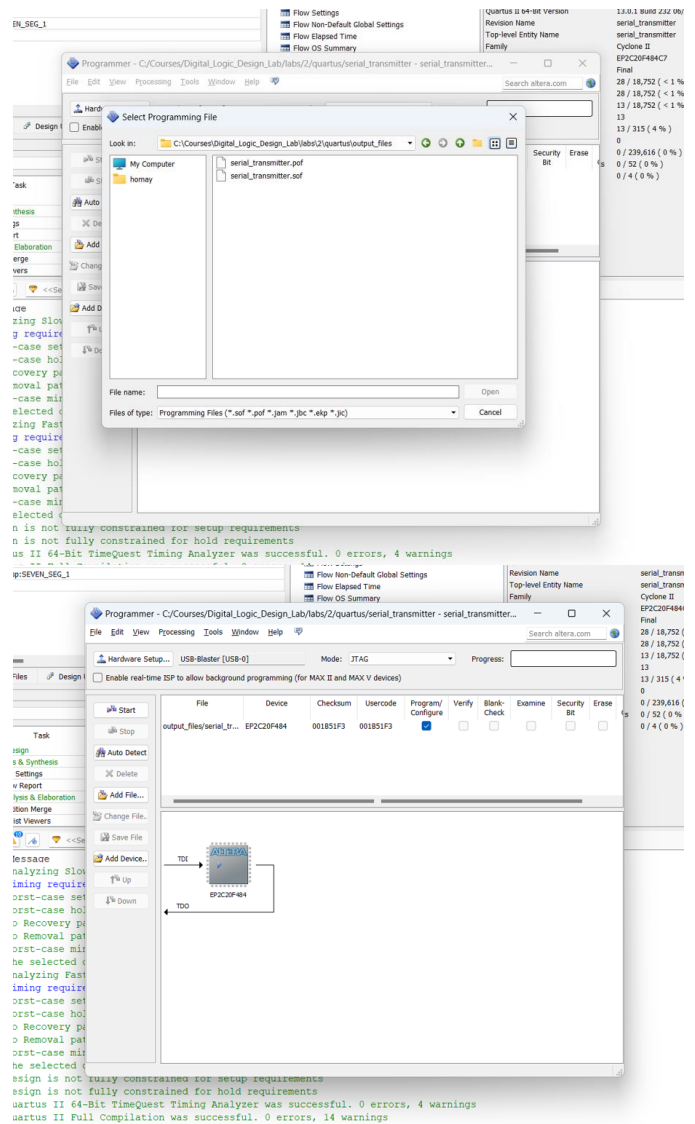

To apply serial input, we pushed the corresponding push-button for the serIn input and then pressed the ClkPB push button once.

 


Fig.4 reset before starting

 


Fig.6 3rd number received

 


Fig.5 sequence is detected

 


Fig.7 8th number received